


Q1

4 NODES : 1 REFERENCE NODE  $V_{REF} = 0V$   
 1 TRIVIAL NODE  $V_S = 10V$   
 1 NODE, NO NEED TO CALC  $V_L$   
 1 NODE, CALC  $V_C = ?$

ALTERNATIVELY, TRANSFORM INTO  
CURRENT SOURCE TO ELIMINATE

2 EQUATIONS W/ 2 UNKNOWNNS  
SOLVE FOR  $V_C$  ONLY

ASSUMED CURRENT DIRECTIONS:

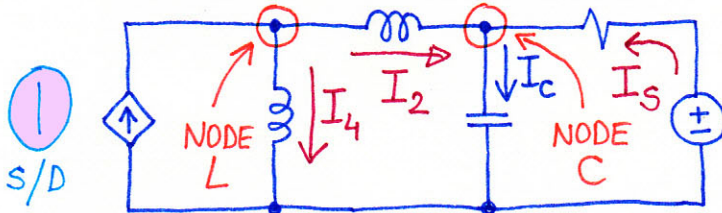

KCL FOR NODE L (2)

$$3I_C = I_4 + I_2$$

KCL FOR NODE C (2)

$$I_2 + I_S = I_C$$

CURRENTS:

$$3I_C = 3 \frac{V_C}{Z_C} = \frac{3}{-j1} V_C = j3V_C \quad (1)$$

$$I_4 = \frac{V_L}{Z_{L4}} = \frac{1}{j4} V_L = -j0.25 V_L \quad (1)$$

$$I_2 = \frac{V_L - V_C}{Z_{L2}} = \frac{1}{j2} (V_L - V_C) = -j0.5 (V_L - V_C) \quad (1)$$

$$I_S = \frac{V_S - V_C}{R} = \frac{1}{8} (10 - V_C) = 0.125 (10 - V_C) \quad (1)$$

$$I_C = \frac{V_C}{Z_C} = \frac{1}{-j1} V_C = jV_C \quad (0.67)$$

PLUG IN CURRENTS  
IN KCL EQUATIONS

$$j3V_C = -j0.25 V_L - j0.5 (V_L - V_C) = -j0.25 V_L - j0.5 V_L + j0.5 V_C$$

(2) EQ.#1  $j2.5 V_C + j0.75 V_L = 0$  EQ.#1  $\Rightarrow V_L = \frac{-j2.5 V_C}{j0.75} = -\frac{10}{3} V_C$

$$-j0.5 (V_L - V_C) + 0.125 (10 - V_C) = jV_C$$

$$-j0.5 V_L + j0.5 V_C + 1.25 - 0.125 V_C - jV_C = 0$$

$$(-0.125 - j0.5) V_C - j0.5 V_L = -1.25 \quad / \cdot (-1)$$

(2) EQ.#2  $(0.125 + j0.5) V_C + j0.5 V_L = 1.25$  EQ.#2

$$(0.125 + j0.5) V_C - j0.5 \cdot \frac{10}{3} V_C = 1.25$$

$$0.125 V_C + j0.5 V_C - j\frac{5}{3} V_C = 1.25$$

$$0.125 V_C - j\frac{3.5}{3} V_C = 1.25$$

FINAL SOLUTION

$$V_C = \frac{1.25}{0.125 - j\frac{3.5}{3}} = \frac{1.25 \cdot 0.125 + j\frac{1.25 \cdot 3.5}{3}}{0.125^2 + (\frac{3.5}{3})^2} = 0.1135 + j1.06 V$$

Q2


$$V_{s1} = 6 \sin(3t) = 6 \cos(3t - 90^\circ) \Rightarrow V_{s1} = 6 \angle -90^\circ \text{ V}$$

$$V_{s2} = 10 \cos(3t) \Rightarrow V_{s2} = 10 \text{ V} \quad \leftarrow \text{TRANSFORM SIN} \rightarrow \text{COS} \quad (2)$$

$$\omega = 3 \frac{\text{rad}}{\text{s}} \quad \leftarrow \text{READ OUT } \omega \quad (1)$$

$$\Rightarrow R = 2 \Omega ; X_L = \omega L = 3 \cdot 2 = 6 \Omega ; X_C = -\frac{1}{\omega C} = -\frac{1}{3 \cdot 0.333} = -1 \Omega \quad (1)$$

THUS THE CIRCUIT IS:

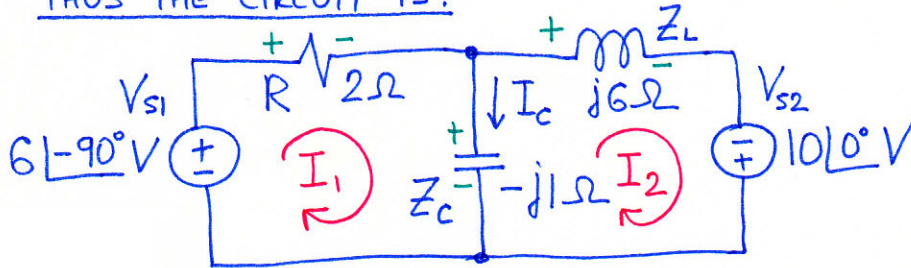

DESIGNATE  
VOLTAGES  
AND  
MESH CURRENTS

(2)

$$I_c \text{ IS REAL (ACTUAL) CURRENT: } I_c = I_1 - I_2 \quad (1)$$

$$\left\{ \begin{array}{l} \text{KVL LOOP 1: } -V_{s1} + RI_1 + Z_C(I_1 - I_2) = 0 \\ \text{KVL LOOP 2: } -V_{s2} - Z_C(I_1 - I_2) + Z_L I_2 = 0 \end{array} \right. \quad \begin{array}{l} (2) \text{ EQ. \#1} \\ (2) \text{ EQ. \#2} \end{array}$$

$$\left\{ \begin{array}{l} 1: 6 \angle -90^\circ = 2I_1 - jI_1 + jI_2 = (2 - j1)I_1 + jI_2 \\ 2: 10 \angle 0^\circ = jI_1 - jI_2 + j6I_2 = j1 \cdot I_1 + j5I_2 \end{array} \right. \Rightarrow$$

$$\left\{ \begin{array}{l} 1: 6 \angle -90^\circ = -j6 = (2 - j1)I_1 + j(-\frac{I_1}{5} - j2) \\ -j6 = (2 - j1)I_1 - j\frac{1}{5}I_1 + 2 \end{array} \right. \quad \left/ \quad I_2 = \frac{10 - jI_1}{j5} = -\frac{I_1}{5} - j2 \quad (0.67)$$

SOLVE

$$-2 - j6 = (2 - j1.2)I_1$$

$$\hookrightarrow I_1 = \frac{-2 - j6}{2 - j1.2} \cdot \frac{2 + j1.2}{2 + j1.2} = \frac{-4 + 7.2 - j2.4 - j12}{2^2 + 1.2^2} = \frac{3.2 - j14.4}{5.44}$$

$$I_1 = 0.5882 - j2.647 \text{ A} \quad (1)$$

$$\begin{aligned} 2: I_2 &= -\frac{I_1}{5} - j2 = -0.2(0.5882 - j2.647) - j2 \\ &= -0.11764 + j0.5294 - j2 \\ &= -0.11764 - j1.4706 \text{ A} \quad (1) \end{aligned}$$

FINALLY:


$$I_c = I_1 - I_2 = 0.5882 - j2.647 + 0.11764 + j1.4706$$

$$I_c = 0.70584 - j1.1764 \text{ A} \quad (2) \text{ FINAL SOLUTION}$$



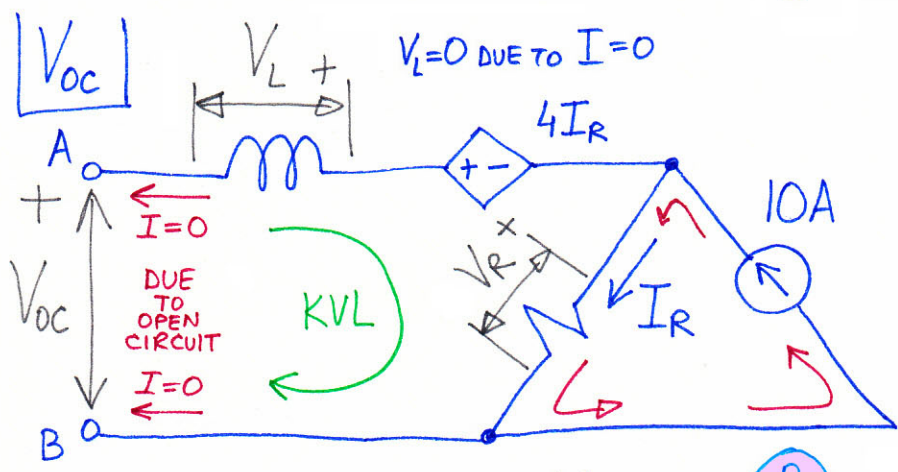Q3

CIRCUIT CONTAINS DEPENDENT SOURCE  
⇒ MUST FIND BOTH  $V_{oc}$  &  $I_{sc}$  (1)




$I_R = 10A$  (1)  
CIRCULATING CURRENT  
 $V_R = I_R \cdot R$   
 $= 10A \cdot 2\Omega$   
 $= 20V$  (1)

KVL:  $-V_{oc} - V_L + 4I_R + V_R = 0$  (2)

$V_{oc} = -0 + 4 \cdot 10 + 20 \Rightarrow V_{oc} = 60V$

$I_{sc}$  REDRAW CIRCUIT:

$V_{TH} = V_{oc} = 60V$  (2)

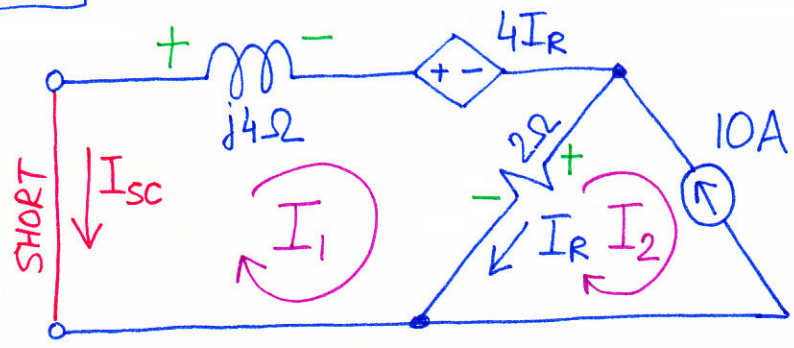

$I_2 = -10A$  ✓ (1)  
 $I_R = I_1 - I_2$   
 $= I_1 - (-10A)$   
 $= I_1 + 10A$  (1)

CANNOT USE CURRENT DIVIDER DUE TO (DEPENDENT) SOURCE. (1)  
USE MESH CURRENTS:

KVL LOOP 1:  $+Z_L I_1 + 4I_R + R I_R = 0$  (2) KVL EQUATION

$j4I_1 + 4(I_1 + 10) + 2(I_1 + 10) = 0$

$j4I_1 + 6I_1 + 60 = 0$


$(6 + j4)I_1 = -60$

THUS  $I_1 = \frac{-60}{6 + j4} \cdot \frac{6 - j4}{6 - j4} = \frac{-360 + j240}{36 + 16} = -\frac{90}{13} + j\frac{60}{13} A$

$I_{sc} = -I_1 = \frac{90}{13} - j\frac{60}{13} A$  (2)

$Z_{TH} = \frac{V_{oc}}{I_{sc}} = \frac{60}{\frac{90}{13} - j\frac{60}{13}} = \frac{6 \cdot 13}{9 - j6} \cdot \frac{9 + j6}{9 + j6} = \frac{702 + j468}{9^2 + 6^2} = 6 + j4\Omega$

$Z_{TH} = 6 + j4\Omega$  (2)

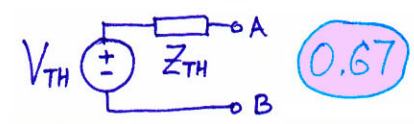

Q4

PERIOD  $T = 6\text{ s}$  <sup>(2)</sup>  $v(t) = \begin{cases} -4\text{V} & 0 \leq t < 3 \\ 2\text{V} & 3 \leq t < 6 \end{cases}$  <sup>(2)</sup> CONSTANT VALUE IN EACH SEGMENT

$$V_{\text{RMS}} = \sqrt{\frac{1}{T} \int_0^T v^2(t) dt} = \sqrt{\frac{1}{6} \left( \int_0^3 (-4)^2 dt + \int_3^6 2^2 dt \right)}$$

$$= \sqrt{\frac{1}{6} \left( 16 \cdot t \Big|_0^3 + 4 \cdot t \Big|_3^6 \right)} = \sqrt{\frac{1}{6} (16 \cdot 3 + 4(6-3))}$$

$$= \sqrt{\frac{1}{6} (48 + 12)} = \sqrt{\frac{60}{6}} = \sqrt{10} \Rightarrow \boxed{V_{\text{RMS}} = 3.16\text{ V}}$$

Q5

SERIES RLC RESONANT CIRCUIT

a) RESONANT FREQUENCY:  $f_0 = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{4 \cdot 10^{-3} \cdot 4 \cdot 10^{-9}}} = \frac{1}{8\pi} \cdot 10^6\text{ Hz}$

THUS  $f_0 = 39.8\text{ kHz}$  <sup>(1.67)</sup>

QUALITY FACTOR:  $Q = \frac{1}{R} \sqrt{\frac{L}{C}} = \frac{1}{4} \sqrt{\frac{4 \cdot 10^{-3}}{4 \cdot 10^{-9}}} = \frac{10^3}{4} \Rightarrow \boxed{Q = 250}$  <sup>(1.5)</sup>

BANDWIDTH:  $B = \frac{f_0}{Q} = \frac{39.8\text{ kHz}}{250} = 159.155\text{ Hz} \Rightarrow \boxed{B = 159.2\text{ Hz}}$  <sup>(1.5)</sup>

b) HALF-POWER FREQUENCIES

$$f_{\text{LOW}} = f_0 \left[ -\frac{1}{2Q} + \sqrt{\left(\frac{1}{2Q}\right)^2 + 1} \right] = f_0 \left[ -\frac{1}{500} + \sqrt{\left(\frac{1}{500}\right)^2 + 1} \right] = f_0 \cdot 0.998$$

$\uparrow$  39.8 kHz

$\Rightarrow \boxed{f_{\text{LOW}} = 39.7204\text{ kHz}}$  <sup>(2)</sup>

$B = f_{\text{HIGH}} - f_{\text{LOW}} \Rightarrow f_{\text{HIGH}} = f_{\text{LOW}} + B = 39,720.4 + 159.2$

$\Rightarrow \boxed{f_{\text{HIGH}} = 39.8796\text{ kHz}}$  <sup>(1)</sup>

c) CURRENT MAGNITUDE @ RESONANCE

$Z_L + Z_C = 0 \Rightarrow I = \frac{V}{R} = \frac{2V_{\text{RMS}}}{4\Omega} \Rightarrow \boxed{I = 500\text{ mA}_{\text{RMS}}}$  <sup>(3)</sup>

d)  $\bar{V}_C$  &  $\bar{V}_L$


IF  $\bar{V}_S$  IS IN REFERENCE  $\Rightarrow \bar{V}_C = Q\bar{V}_S \angle -90^\circ = 500 \angle -90^\circ V_{\text{RMS}}$  <sup>(1.5)</sup>  
 $\bar{V}_L = Q\bar{V}_S \angle 90^\circ = 500 \angle 90^\circ V_{\text{RMS}}$  <sup>(1.5)</sup>

e) 10 TIMES LOWER Q

$Q = \frac{1}{R} \sqrt{\frac{L}{C}} \sim \frac{1}{\sqrt{C}}$  CAPACITANCE MUST INCREASE 100 TIMES  $\boxed{C_{\text{NEW}} = 0.4\mu\text{F}}$  <sup>(3)</sup>



Q6

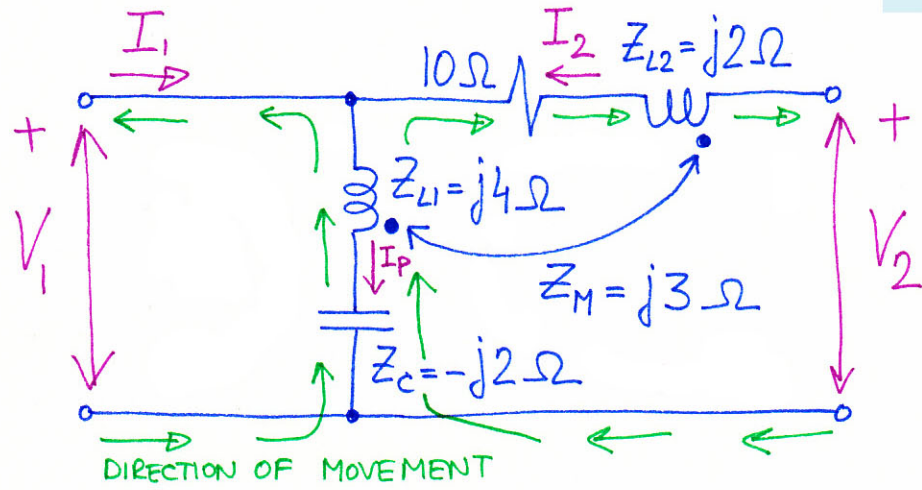

$I_p$  FLOWS OUT OF DOT OF  $L_1$   
 $I_2$  FLOWS INTO DOT OF  $L_2$   
 $I_p = I_1 + I_2$   
 HINT ON WRITING EQUATIONS TUTORIAL #10, PROBLEM 6

ASSUME STANDARD 2-PORT NETWORK DIRECTIONS FOR  $I_1$  AND  $I_2$ .  
 $Z$  PARAMETER EQUATIONS:

$$\begin{aligned} V_1 &= Z_{11} I_1 + Z_{12} I_2 \quad (2) \\ V_2 &= Z_{21} I_1 + Z_{22} I_2 \end{aligned}$$

WRITE EQUATIONS FOR  $V_1$  AND  $V_2$  ACCORDING TO RULES FOR MAGNETICALLY COUPLED INDUCTORS:

$$\begin{aligned} V_1 &= \underbrace{+Z_c I_p}_{\text{CAP}} + \underbrace{Z_{L1} I_p}_{\text{SELF}} - \underbrace{Z_M I_2}_{\text{MUTUAL}} \quad (4) \quad \text{CURRENTS DO NOT MATCH (OPPOSITE SIGN FROM SELF TERM)} \\ &= (Z_c + Z_{L1}) I_p - Z_M I_2 \\ &= (-j2 + j4)(I_1 + I_2) - j3 I_2 \\ &= j2 I_1 + j2 I_2 - j3 I_2 = \underbrace{(j2)}_{Z_{11}} I_1 + \underbrace{(-j1)}_{Z_{12}} I_2 \end{aligned}$$

$$\begin{aligned} V_2 &= \underbrace{+Z_c I_p}_{\text{CAP}} + \underbrace{Z_{L1} I_p}_{\text{SELF L1}} - \underbrace{Z_M I_2}_{\text{MUTUAL (I2 REMOTE)}} + \underbrace{R I_2}_{\text{R}} + \underbrace{Z_{L2} I_2}_{\text{SELF L2}} - \underbrace{Z_M I_p}_{\text{MUTUAL (Ip REMOTE)}} \quad (6) \\ &= (Z_c + Z_{L1} - Z_M) I_p + (R - Z_M + Z_{L2}) I_2 \\ &= (-j2 + j4 - j3)(I_1 + I_2) + (10 - j3 + j2) I_2 \\ &= -j1 I_1 - j1 I_2 + (10 - j1) I_2 \\ &= \underbrace{(-j1)}_{Z_{21}} I_1 + \underbrace{(10 - j2)}_{Z_{22}} I_2 \end{aligned}$$

THUS  $Z$  MATRIX IS:

$$Z = \begin{bmatrix} j2 & -j1 \\ -j1 & 10 - j2 \end{bmatrix}$$

0.67

Q7

TRANSFER FUNCTION: (APPLY VOLTAGE DIVIDER RULE)

$$\bar{H} = \frac{\bar{V}_{OUT}}{\bar{V}_{IN}} = \frac{Z_R}{Z_R + Z_L} = \frac{R}{R + j\omega L} \cdot \frac{\frac{1}{R}}{\frac{1}{R}} = \frac{1}{1 + j\omega \frac{L}{R}} \quad (2)$$

PLUG IN R AND L VALUES:

$$\omega_p = \frac{R}{L} = \frac{10 \Omega}{0.1 \text{mH}} = 100 \text{k} \frac{\text{rad}}{\text{s}} \quad (2)$$


$$\omega_p = \frac{R}{L}$$

STANDARD FORM:

$$H(j\omega) = \frac{1}{1 + j \frac{\omega}{\omega_p}} = \frac{1}{1 + j \frac{\omega}{100\text{k}}} \quad (2.67)$$

$K_0 = 1$   
"EMPTY" NUMERATOR  
1<sup>ST</sup> ORDER TERM IN DENOMINATOR  
CORNER FREQUENCY  $\omega_p$

a) MAGNITUDE PLOT (4)

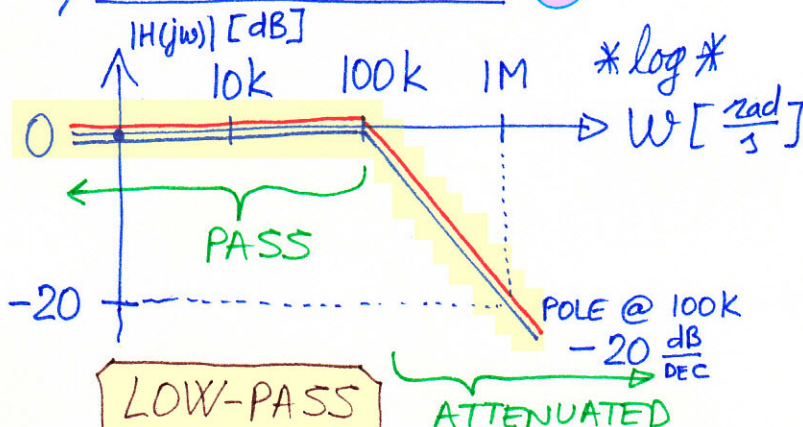


ONLY ONE COMPONENT.  
FINAL PLOT IS THE SAME AS 1<sup>ST</sup> ORDER TERM PLOT.

**LOW-PASS FILTER** (2)

ANSWER TO b)

PHASE PLOT (4)

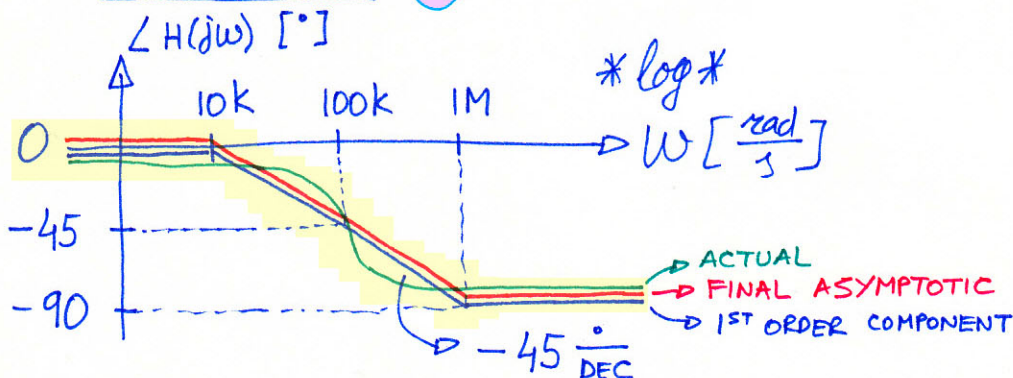

ACTUAL  
FINAL ASYMPTOTIC  
1<sup>ST</sup> ORDER COMPONENT



Produced by:  
**Sasha Jakovljevic**  
[eeSasha.com](http://eeSasha.com)

